

IBM ASSIGNMENT- I

TEAM ID : PNT2022TMID26661


NAME : SHANMUGAM.V

ROLL NO : 212919106080

Create a circuit with Piezo alarm, PIR Sensor, TMP Sensor with below functionalities:

1. Alarm should sound in one manner if temp is above 60C
2. Alarm should sound with another frequency if motion is detected in PIR Sensor.

CIRCUIT LAYOUT:

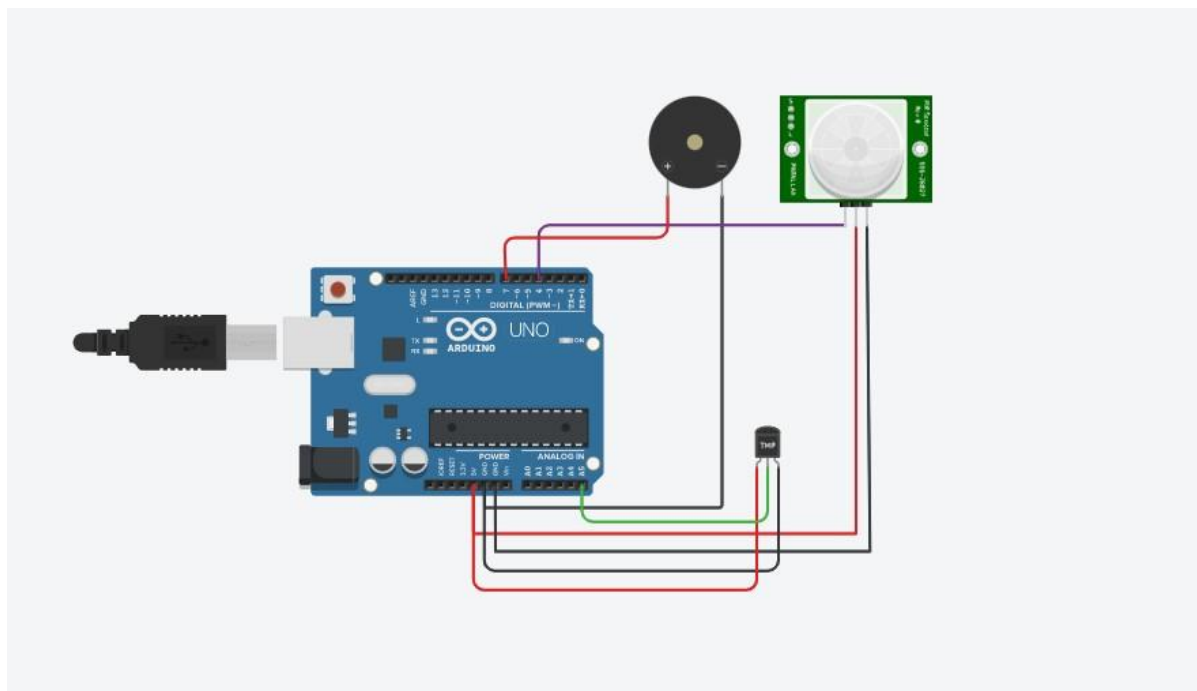

CODE:

```
// C++ code
//
void setup()
{
  Serial.begin (9600);
  pinMode(4, INPUT);
  pinMode(7,OUTPUT);
  pinMode(A5,INPUT);
}

void loop()
{
  int motion = digitalRead(4);
  if (motion==1){
    Serial.println("Motion detected");
    tone (7,200);
    delay(350);
  }
  else{
    Serial.println("No Motion");
    noTone(7);
  }
}
{
  double data=analogRead(A5);
  double n=data/1024;
  double volt=n*5;
  double off=volt-0.5;
  double temperature=off*100;
  if (temperature>59.99){
    Serial.print("Temperature data:");
    Serial.println(temperature);
    tone(7,1000);
    delay(350);
  }
}
```


```

else
  Serial.print("Temperature data: ");
  Serial.println(temperature);
  noTone(7);
}
}

```

OUTPUT:

PASSIVE INFRARED SENSOR:

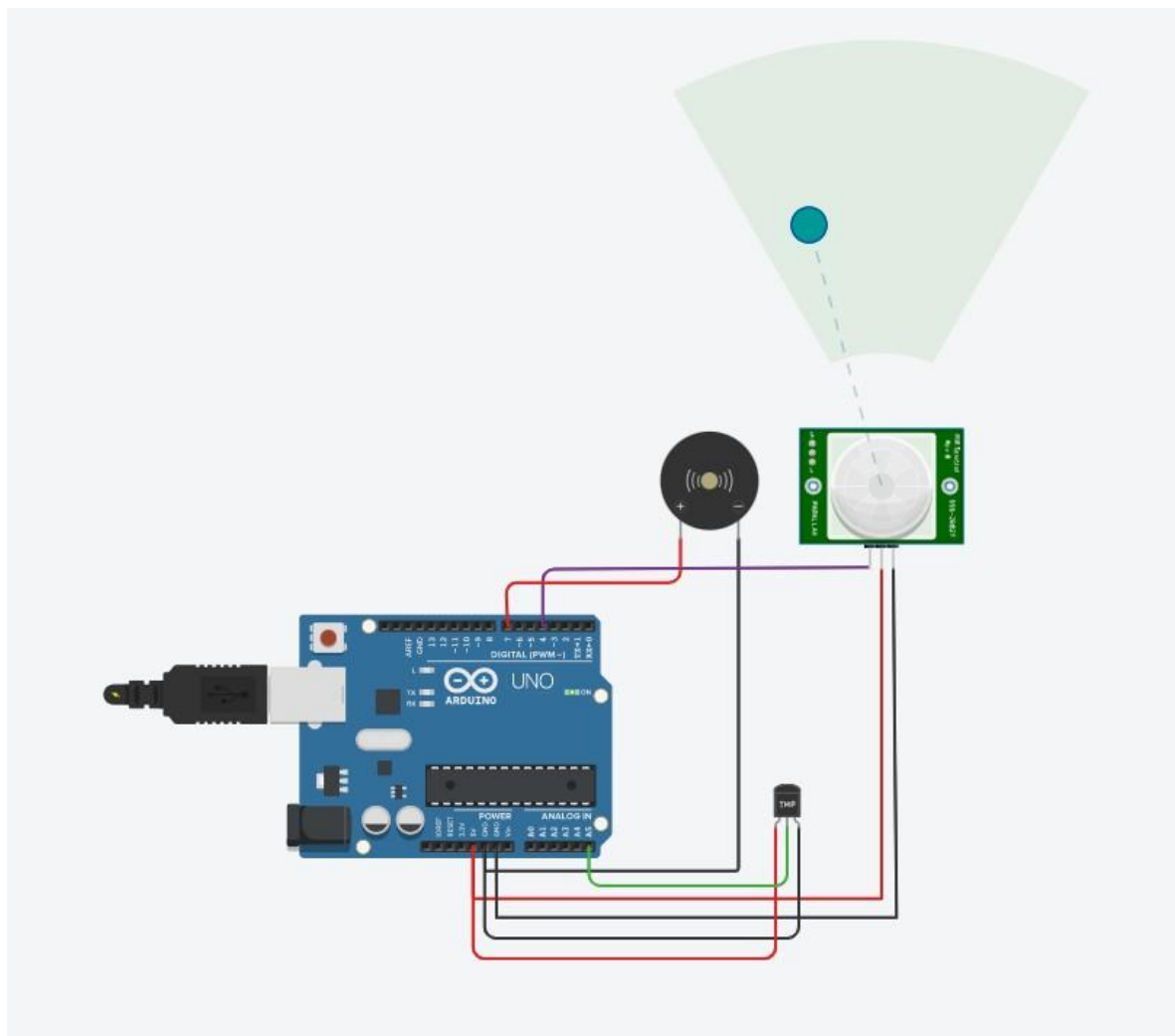

TEMPERTURE SENSOR (AT 60°C):

