IBM ASSIGNMENT-I

TEAM ID: PNT2022TMID26661


NAME : PAUL.V

ROLL NO: 212919106062

Create a circuit with Piezo alarm, PIR Sensor, TMP Sensor with below functionalities:

- 1.Alarm should sound in one manner if temp is above 60C
- 2. Alarm should sound with another frequency if motion is detected in PIR Sensor.

CIRCUIT LAYOUT:

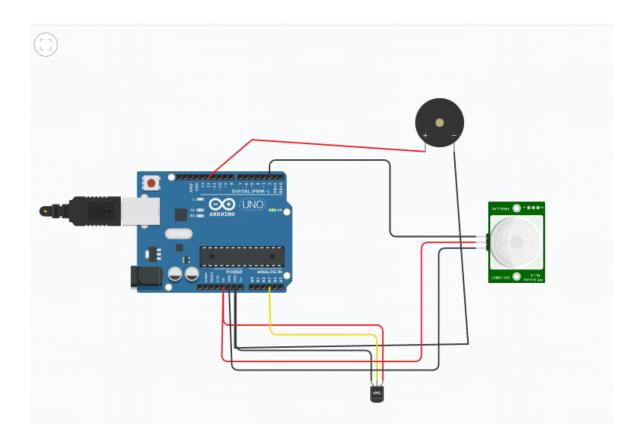


CODE:

```
void setup()
{
 Serial.begin (9600);
 pinMode(2, INPUT);
 pinMode(12,OUTPUT);
 pinMode(A3,INPUT);
}
void loop()
 int motion = digitalRead(2);
 if (motion==1){
  Serial.println("Motion detected");
  tone (12,20000);
  delay(500);
 }
 else{
  Serial.println("No Motion");
  noTone(12);
 }
 double data=analogRead(A3);
 double n=data/1024;
 double volt=n*5;
 double off=volt-0.5;
 double temperature=off*100;
```

```
if (temperature>59.99){
    Serial.print("Temperature data:");
    Serial.println(temperature);
    tone(12,10000);
    delay(500);
}
else
    Serial.print("Temperature data: ");
    Serial.println(temperature);
    noTone(12);
}
```

OUTPUT:

PASSIVE INFRARED SENSOR:

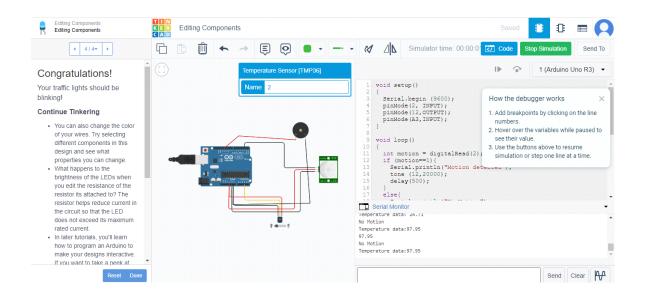

TEMPERTURE SENSOR (60 C):

